
ELECTRONICS FOR ENGINEERS

***Reference articles, charts, and graphs
from Electronics magazine***

Edited by
JOHN MARKUS
and
VIN ZELUFF
Associate Editors, Electronics

FIRST EDITION
FIFTH IMPRESSION

McGRAW-HILL BOOK COMPANY, INC.
NEW YORK AND LONDON
1945

ELECTRONICS FOR ENGINEERS

COPYRIGHT, 1945, BY THE
MCGRAW-HILL BOOK COMPANY, INC.

PRINTED IN THE UNITED STATES OF AMERICA

*All rights reserved. This book, or
parts thereof, may not be reproduced
in any form without permission of
the publishers.*

Preface

ENGINEERS are busy people. They invent all manner of short cuts for themselves; they condense much information into the small space of graphs and charts. In many cases they share this information with other engineers by publishing it in the technical press.

Monthly magazines are not exactly convenient for reference—even in bound volumes—when they have accumulated for a few years. In an earnest attempt to solve this problem for one McGraw-Hill publication—*Electronics*—the editors of this book have gone through the complete files of the magazine from the first issue (April, 1930), and from this wealth of technical data have selected 142 articles, reference sheets, charts, and graphs that have been in greatest demand for their reference value. All this material has been carefully checked, edited, and condensed where desirable to put it into the best possible form for presentation in a book. The individual papers were then grouped into chapters for convenient reference to make the book practically self-indexing.

Designers, builders, and users of electronic equipment and component parts will find here, under the headings of their respective fields of interest, the equations and other data so badly needed yet often so hard to find. One article alone, available when needed, can justify a place for this book on an engineer's desk.

The editorial staff of *Electronics* takes pride in the repeated requests that have come in for tear sheets or photostats and is glad that these articles are now available in handy and economical form between the covers of one book.

The engineer authors whose works appear in this volume deserve congratulations for their permanent contributions to the art and industry of electronics.

KEITH HENNEY,
Editor, *Electronics*.

NEW YORK, N. Y.,
October, 1945.

Contents

			PAGE
PREFACE			V
I. A-F IMPEDANCE-MATCHING NETWORKS			
	<small>DATE PUBLISHED</small>	<small>AUTHOR</small>	
Design Charts for Dissymmetrical T Pads	<i>July, 1943.</i>	EDWIN Y. WEBB, JR.	1
Design Procedure for Dissymmetrical T and π Attenuators	<i>Aug., 1942.</i>	P. M. HONNELL	3
Multiple-circuit Pads	<i>Mar., 1937.</i>	FREDERICK WHEELER.	6
Forty Commonly Used Pads	<i>Apr., 1940.</i>	AARON SHELTON	9
Universal Network Design Chart	<i>Mar., 1935.</i>	A. JAMES EBEL.	10
Attenuator-design Formulas	<i>Nov., 1941.</i>	DAWKINS ESPY.	11
II. ANTENNAS			
Aircraft Antenna Characteristics	<i>Dec., 1942</i>	PAUL J. HOLMES	17
Design of Two-tower Directional Arrays.	<i>Apr., 1936.</i>	E. A. LAPORT.	19
Directional Radiation Patterns of Two-element Vertical Antenna Arrays.	<i>Apr., 1936.</i>	A. JAMES EBEL.	23
Antenna Power Divider	<i>July, 1944.</i>	EARLE TRAVIS	25
Computing Performance of Two-tower Directional Arrays	<i>Aug., 1937.</i>	A. R. RUMBLE	26
Voltage Gain Charts for Two-antenna Arrays.	<i>Feb., 1940</i>	W. S. DUTTERA.	29
Field Strength Prediction Charts Based on Sommerfeld's Formula.	<i>Sept., 1936.</i>	WILLIAM A. FITCH	30
Radiation Chart for Vertical Antennas.	<i>July, 1939.</i>	L. J. GIACOLETTO.	32
Design Procedure for Ground Plane Antennas	<i>Aug., 1943.</i>	H. W. HASENBECK	34
Design Chart for Antenna Phase-shifting Networks	<i>Oct., 1942</i>	W. S. DUTTERA.	37
Phasing Networks for Broadcast Arrays	<i>June, 1944.</i>	C. RUSSELL COX	40
Calculating Broadcast-station Coverage	<i>May, 1936.</i>	RAYMOND F. GUY.	45
Radial Ground System Chart.	<i>Jan., 1938.</i>	GEORGE H. BROWN.	47
III. AUDIO AMPLIFIERS			
Resistance-coupled Amplifier Design Charts	<i>Aug., 1936.</i>	GLENN KOEHLER.	48
Design of Class A Push-pull Amplifiers.	<i>June, 1937.</i>	E. W. HOUGHTON.	50
Design of Class B and AB Output Transformers	<i>Feb., 1936</i>	GLENN KOEHLER.	52
Cathode-follower Calculations	<i>Oct., 1944</i>	HUMBERT P. PACINI.	55
Harmonic Analysis of Overbiased Amplifiers	<i>Mar., 1944.</i>	ULRICH R. FURST.	56
IV. AUDIO-CIRCUIT DESIGN			
Bass-compensation Design Chart	<i>Oct., 1937</i>	P. A. D'ORIO and R. DE COLA.	58
Simple RC Equalizer Networks.	<i>Feb., 1944</i>	C. J. MERCHANT	60
Universal 15-channel Tone Control for Audio Amplifiers.	<i>Aug., 1943.</i>	PAUL H. THOMSEN	63
Computing Reactive Attenuation.	<i>May, 1936.</i>	P. F. BECHBERGER	65
Time Delay in Resistance-capacitance Circuits	<i>Feb., 1937</i>	E. W. KELLOGG and W. D. PHELPS.	67
V. CAPACITORS			
Rounded-edge Capacitor Plate Design.	<i>Oct., 1944</i>	SAMUEL SABAROFF	3
V-h-f Behavior of Capacitors.	<i>Mar., 1944.</i>	E. L. HALL.	76
Capacitor-discharge Chart	<i>June, 1940.</i>	LOUIS HANOPOL	80
Capacitor Charge-discharge Nomograph	<i>Sept., 1937.</i>	J. B. HOAG.	82
Capacitor-lead Resonance Chart	<i>Aug., 1939.</i>	R. L. HASKINS	83
Resonance Chart for Mica Capacitors	<i>Mar., 1944.</i>	A. P. GREEN and C. T. McCOMB.	85
Power Factor Correction Charts	<i>May, 1944.</i>	HARRY HOLUBOW.	86
Temperature Compensation of Tuned Circuits	<i>Apr., 1944.</i>	HERBERT SHERMAN.	88
Determining Frequency Stability of Tuned Circuits.	<i>Feb., 1944</i>	G. V. ELTGROTH	89
VI. CATHODE-RAY TUBES			
Characteristics of Phosphors for Cathode-ray Tubes.	<i>Dec., 1938</i>	L. B. HEADRICK	92
Photographing Patterns on Cathode-ray Tubes.	<i>Feb., 1944</i>	RUDOLPH FELDT	93

VII. COAXIAL LINES

	DATE PUBLISHED	AUTHOR	PAGE
Design of Terminations for Concentric Lines	Dec., 1936	CARL G. DIETSCH	99
Q-factor Charts for Unloaded Concentric Transmission Lines	Sept., 1943	R. C. MIEDKE	103
Impedance Determinations of Eccentric Lines	Feb., 1942	GEORGE H. BROWN	105
Graph of Impedance of Eccentric-conductor Cable	Feb., 1942	W. J. BARCLAY and K. SPANGENBERG	106
Measurement of H-f Lines	Apr., 1938		107

VIII. ELECTRONIC HEATING

Electronic Heating Design Chart	Apr., 1944	C. V. FIELDS	110
Surface Hardening of Metals	July, 1944	H. C. GILLESPIE	112
Power Equations for Dielectric Heating	Aug., 1943	CYRIL N. HOYLER	114
Design Chart for R-f Heat-treatment Generators	Sept., 1941	EUGENE MITTELMAN	116
Design Data for Induction Heating Coils	Aug., 1944	GEORGE H. BROWN	117
Magnetic Field Equations for Induction Heating Coils	June, 1944	GEORGE H. BROWN	123

IX. FILTERS

Constant-K Filter-design Chart	Aug., 1940	JOHN BORST	127
M-derived Filter-design Chart	Oct., 1940	JOHN BORST	129
Filter-conversion Chart	Nov., 1940	JOHN BORST	130

X. INDUSTRIAL CONTROL

Design of Electronic Control Circuits	Aug., 1943	W. A. SCHWARZMANN	133
Capacitor Discharge Welding Systems	May, 1944	H. KLEMPERER	136
Grid Control of Industrial Gas-filled Tubes	June, 1944	W. D. COCKRELL	140

XI. IRON-CORE TRANSFORMERS AND CHOKES

Notes on Iron-core Transformer Design	Feb., 1944	E. B. HARRISON	145
Design of Audio Reactors for D-c Service	Sept., 1936	REUBEN LEE	147

XII. MATHEMATICS

Amplification Factor Chart	June, 1939	E. R. JERVIS	151
Polar-rectangular and Rectangular-reciprocal Vector Charts	Dec., 1941	PAUL W. KLIPSCH	153
Impedance-conversion Chart	Oct., 1944	PERRY H. WARE	155
Impedance-magnitude and Phase-angle Charts	Jan., 1943	T. C. BLOW	156
Impedance-combining Chart	Mar., 1944	GARY MUFFLY	158
Chart for Equivalent Series and Parallel Circuits	Apr., 1943	R. TOOMBS	161
Equivalent Resistance Chart	Aug., 1938	A. E. TEACHMAN	163
Chart for Determining Square Root of a Complex Number	Aug., 1943	ROBERT G. NISLE	165

XIII. NETWORKS

Pi Networks as Coupled Tank Circuits	Aug., 1944	F. D. SCHOTTLAND	167
Impedance-magnitude and Phase-shift Curves for Linear Networks	Nov., 1942	VITOLD L. EDUTIS	171
Equalizer Design	Apr., 1944	MICHAEL J. DiTORO	174
Evaluating Performance of Symmetrical Four-terminal Networks	Nov., 1942	E. S. PURINGTON	177
Reactance Networks with Resistance Terminations	Jan., 1943	E. S. PURINGTON	181
Low- and High-pass Wave Filter Units	June, 1943	E. S. PURINGTON	185
Band-pass Wave Filters	Sept., 1943	E. S. PURINGTON	189

XIV. OSCILLATORS

Phase-shift Oscillator Design Charts	Nov., 1943	WALTER W. KUNDE	193
Determining Temperature Coefficient of Quartz Crystals	Nov., 1943	NORMAN L. CHALFIN	195

XV. PERMANENT MAGNETS

Permanent-magnet Design	Dec., 1943	EARL M. UNDERHILL	197
Designing Stabilized Permanent Magnets	Jan., 1944	EARL M. UNDERHILL	203
Mechanical Problems of Permanent-magnet Design	Feb., 1944	EARL M. UNDERHILL	207

CONTENTS

ix

XVI. PULSES

	DATE PUBLISHED	AUTHOR	PAGE
Determining Shape and Magnitude of Amplified Pulses	Nov., 1939.	ERIC A. WALKER.	211
Computing Circuit Response to Pulses	July, 1944.	JOHN B. TREVOR	213
Circuit Response to Nonsinusoidal Wave Forms	Oct., 1944	P. T. CHIN	216
Square-wave Harmonic Amplitude Table	May, 1940.	DONALD L. HERR	219
Square Waves for Impedance Measurements	Sept., 1944.	FRANK ROCKETT	220

XVII. RECTIFIERS

Behavior of Half-wave Rectifiers	Sept., 1939.	M. B. STOUT	224
Half-wave Gas Rectifier Circuits	Oct., 1938	C. M. WALLIS	226
Full-wave Rectifier Analysis	Mar., 1940.	C. M. WALLIS	229
Filter Performance Charts for Half-wave Rectifiers	Apr., 1941.	W. K. H. PANOFSKY and C. F. ROBINSON	233
Rectifier Filter Design	June, 1938.	HERBERT J. SCOTT	236
Filter Design for Grid-controlled Rectifiers	Sept., 1944.	HAROLD A. THOMAS	239

XVIII. RELAYS

Choosing Relays for Tube Output Circuits	Aug., 1937.	E. E. GEORGE	243
Design Chart for Sensitive Relays	Oct., 1943	R. T. FISHER	246

XIX. R-F COILS AND TRANSFORMERS

Distributed Capacitance Chart	Mar., 1938.	P. H. MASSAUT	249
Nomogram for Single-layer Coils	Jan., 1937.	CARL P. NACHOD	251
General-purpose Chart for Multilayer Coils	Jan., 1939.	J. E. MAYNARD	253
Simplified Inductance Chart for Multi-layer Coils	Sept., 1942.	E. S. PURINGTON	256
Winding the Universal Coil	Oct., 1936	A. W. SIMON	258
Mutual-inductance Calculations	July, 1937.	DALE POLLACK	261
H-f Inductance Charts	Mar., 1940.	F. C. EVERETT	263
Universal Performance Curves for Tuned Transformers	Feb., 1937	J. E. MAYNARD	264
Double-tuned Transformer Design	Oct., 1944	DAWKINS ESPY	267

XX. R-F IMPEDANCE-MATCHING NETWORKS

R-f Impedance-matching Networks	Jan., 1936.	RALPH P. GLOVER	270
Charts for L-type Impedance-transforming Circuits	Mar., 1942.	PHILLIP H. SMITH	272
Computing R-f Transition Losses	Jan., 1936.	HAROLD A. WHEELER	278

XXI. R-F POWER AMPLIFIERS

R-f Power-amplifier Chart	Dec., 1939	E. H. SCHULZ	281
Power-amplifier Plate Tank Circuits	Nov., 1941.	ARVID B. NEWHOUSE	283
Class B R-f Amplifier Chart	Nov., 1937.	286
Power Efficiency of R-f Power-amplifier Stages	July, 1944.	HARRY STOCKMAN	287
Graphical Determination of Power-amplifier Performance	Dec., 1942	R. I. SARBACHER	291
Analysis of Self-biased Modulated Amplifiers	Apr., 1943.	R. I. SARBACHER	295

XXII. SOUND

Design for Exponential Horns of Square Cross-section	Feb., 1939	GEORGE H. LOGAN	302
Chart of VU-DB Relationships	May, 1939.	FRANK B. HALES	303
DB Ruler for Christmas-tree Patterns on Records	May, 1941.	DON R. KING	304

XXIII. TELEVISION, FREQUENCY MODULATION, AND FACSIMILE

Shunt-peaking Compensation for Video Amplifiers	Jan., 1940.	WILLIAM H. FREEMAN	305
Television Definitions and Design Equations	Mar., 1939.	DONALD G. FINK	307
Influence of Feedback in Video Amplifiers	Sept., 1944.	RICHARD W. CRANE	309
Single-inductor Video Coupling Networks	Sept., 1944.	C. T. McCOMB and A. P. GREEN	311
Frequency-deviation Measurement of F-m Transmitters	Oct., 1941	L. N. HOLLAND and L. J. GIACOLETTO	317
Facsimile Design Chart	Apr., 1941.	RAYMOND R. HAUGH	320

CONTENTS

XXIV. TRANSMISSION LINES

	DATE PUBLISHED	AUTHOR	PAGE
Transmission-line Charts.	July, 1943.	R. F. BAUM	321
Characteristics of Resonant Transmission Lines.	Oct., 1943	J. B. EPPERSON.	324
Transmission-line Calculator	Jan., 1944.	PHILLIP H. SMITH.	326
Impedance Chart for R-f Lines	Dec., 1936	A. E. TEACHMAN	332
Transmission-loss Charts.	June, 1944.	JACK G. ROOF	333
R-f Matching Sections.	Jan., 1941.	A. C. OMBERG	335
Universal Wave Guide Chart.	Dec., 1943	ARTHUR BRONWELL.	336
Skin-effect Charts and Formulas	Feb., 1942	J. R. WHINNERY	338
R-f Resistance of Copper Wire	Feb., 1936	JOHN H. MILLER.	343

XXV. TUBES

Tube Filament and Heater Characteristics.	July, 1944.	CECIL E. HALLER	344
Secondary Electron Radiation	Sept., 1944.	J. H. OWEN HARRIES	349
Open-grid Tubes in Low-level Amplifiers.	Oct., 1944	ROBERT J. MEYER	358
28-volt Operation of Receiving Tubes	Aug., 1944.	C. R. HAMMOND, E. KOHLER and W. J. LATTIN	360

XXVI. TUNED CIRCUITS

Bandwidth Factors for Cascade Tuned Circuits.	July, 1941.	C. E. DEAN	365
Frequency Response of Parallel Resonant Wave Traps.	Aug., 1941.	MYRIL B. REED	367
Narrow Band-pass Filter Performance.	May, 1943.	H. HOLUBOW.	369
Attenuation Charts for Band-pass and Band-rejection Filters	Aug., 1942.	H. HOLUBOW.	372
Band-pass Characteristics	July, 1936.	H. W. JADERHOLM	375
Superheterodyne Oscillator Tracking Chart.	Nov., 1942.	P. C. GARDINER	377

XXVII. WIDE-BAND AMPLIFIERS

Compensated Amplifier Chart	Sept., 1939.	Y. J. LIU and J. D. TRIMMER.	379
Distortion in Compensated Amplifiers.	July, 1940.	J. D. TRIMMER and Y. J. LIU.	381
D-c Amplifier Design Techniques	Mar., 1944.	EDWARD L. GINZTON	384
Thermal Noise in a Parallel RC Circuit	July, 1944.	C. J. MERCHANT	389

Electronics Projects for Engineers | Top Electronics Project Ideas. Electronics projects are becoming increasingly complex with the demand for solutions for everyday problems. Additionally with IoT coming into the mix, electronics projects have taken on a whole different meaning. Below are hand picked projects for electronics engineers. The lists range over Arduino and Raspberry pi among other projects. Electronics projects overview. Electronics Projects for the IoT. Mini Projects. Raspberry Pi Based Electronics Projects.